

Introduction









ACOL2015: Digital Logic And System Design

Abhilash Jindal

Administrivia

- Lectures: M, T, Th. 8-9 am
- Labs/Office hours: T. 5-7 pm
- TA: Satyam Jay
- Textbook: Digital Design by M. Morris Mano, Michael D. Ciletti. 6th Edition

Digital systems are all around us

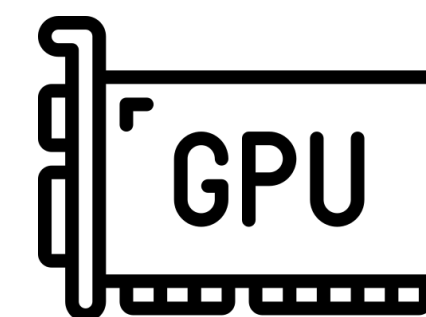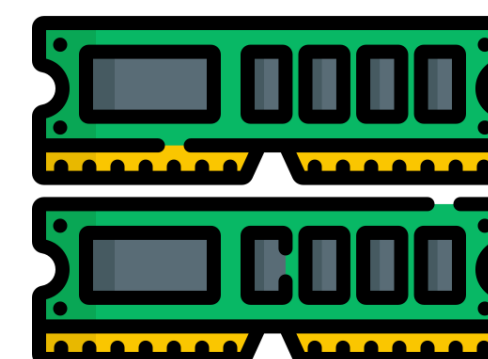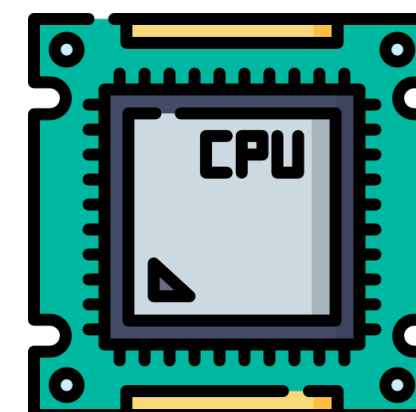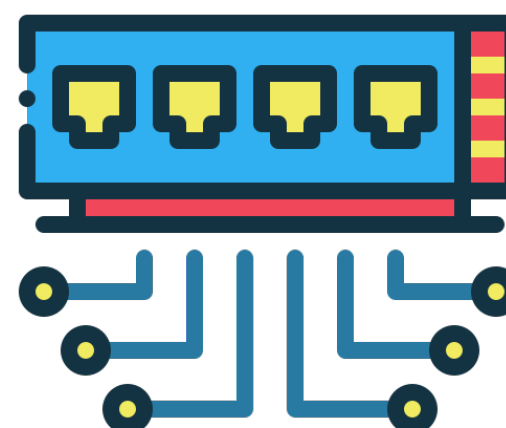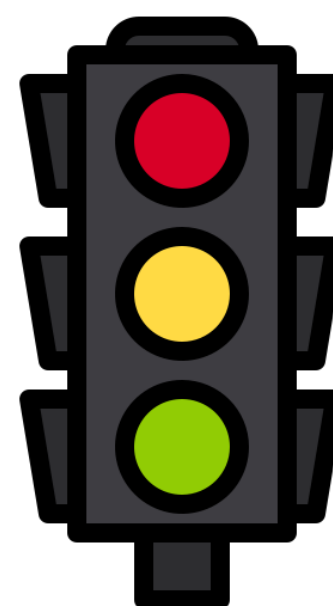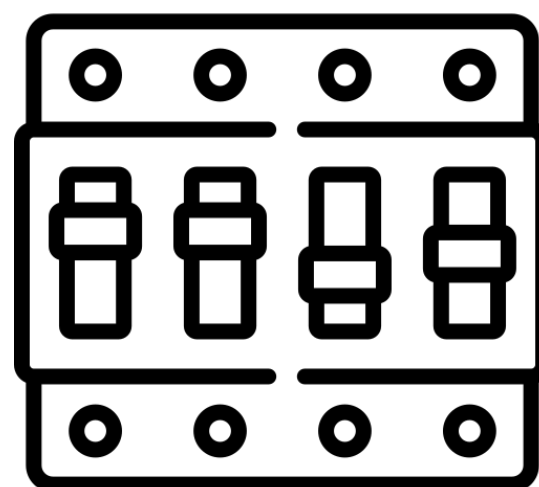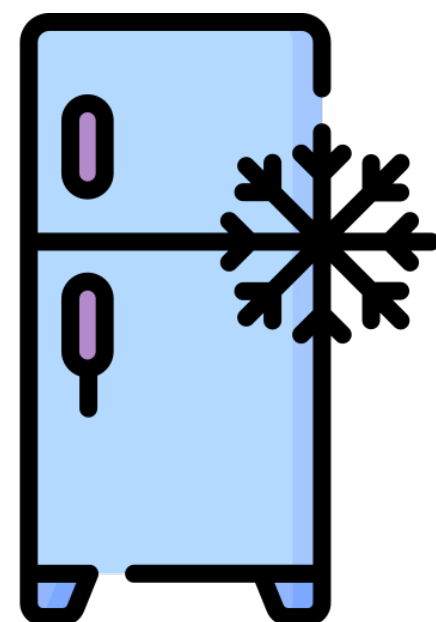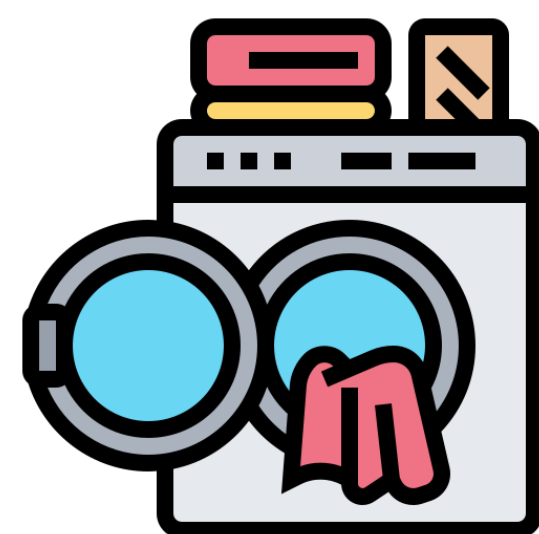

Computer




Special-purpose

General

Digital systems contain circuits to implement some logic

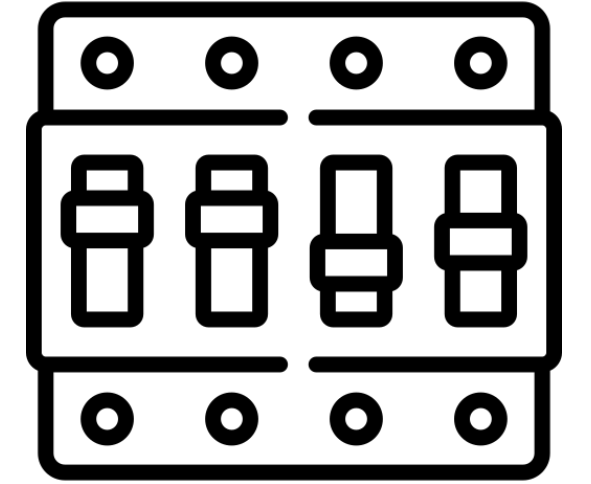
Example: switches

- Turn the light on when any of the four switches are on



Digital systems contain circuits to implement some logic

Example: traffic lights

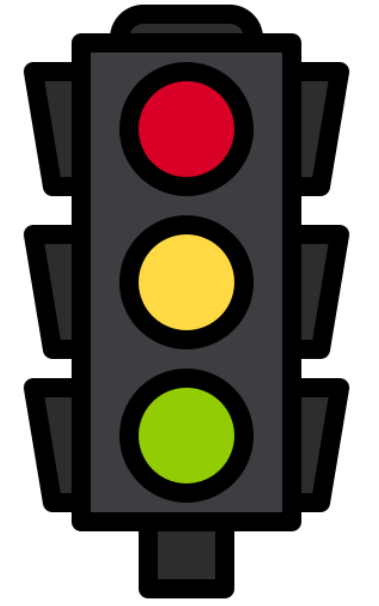

- Loop
 - Wait 1 minute, change light to yellow
 - Wait 10 seconds, change light to green
 - Wait 20 seconds, change light to red

Digital systems contain circuits to implement some logic

Example: washing machine

- ?



Types of circuits

- Combinational Circuit
 - Outputs are a function of only the inputs. They have no *memory*
 - Example: Switches
 - Main building block: Gates
- Sequential Circuit
 - Outputs are a function of inputs and current *state*
 - Example: Traffic lights, Washing machines, CPU
 - Main building block: Gates and Flip flops



Goals

- Build basics of digital logic: Binary number system (Ch 1), Boolean algebra and logic gates (Ch 2), Gate-level minimisation (Ch 3)
- Understand foundations of circuit design: combinational logic (Ch 4), Synchronous sequential logic (Ch 5)
- Use foundations to build circuits: Registers and counters (Ch 6), Memory and programmable logic (Ch 7)
- Learn Verilog (Hardware Description Language) to build circuits

Math Basics

Set

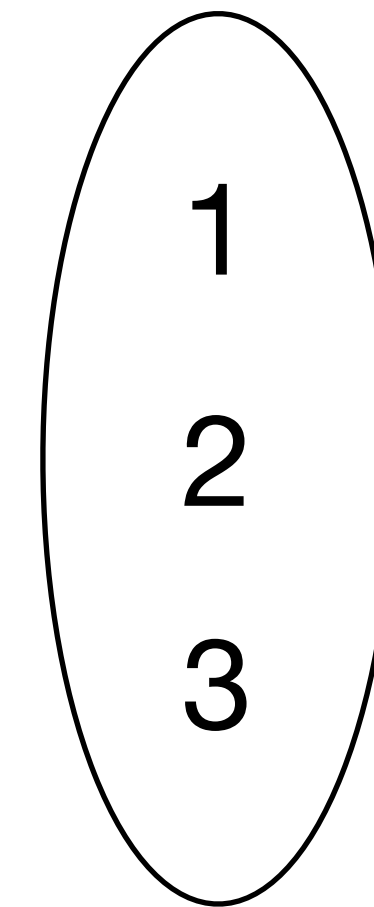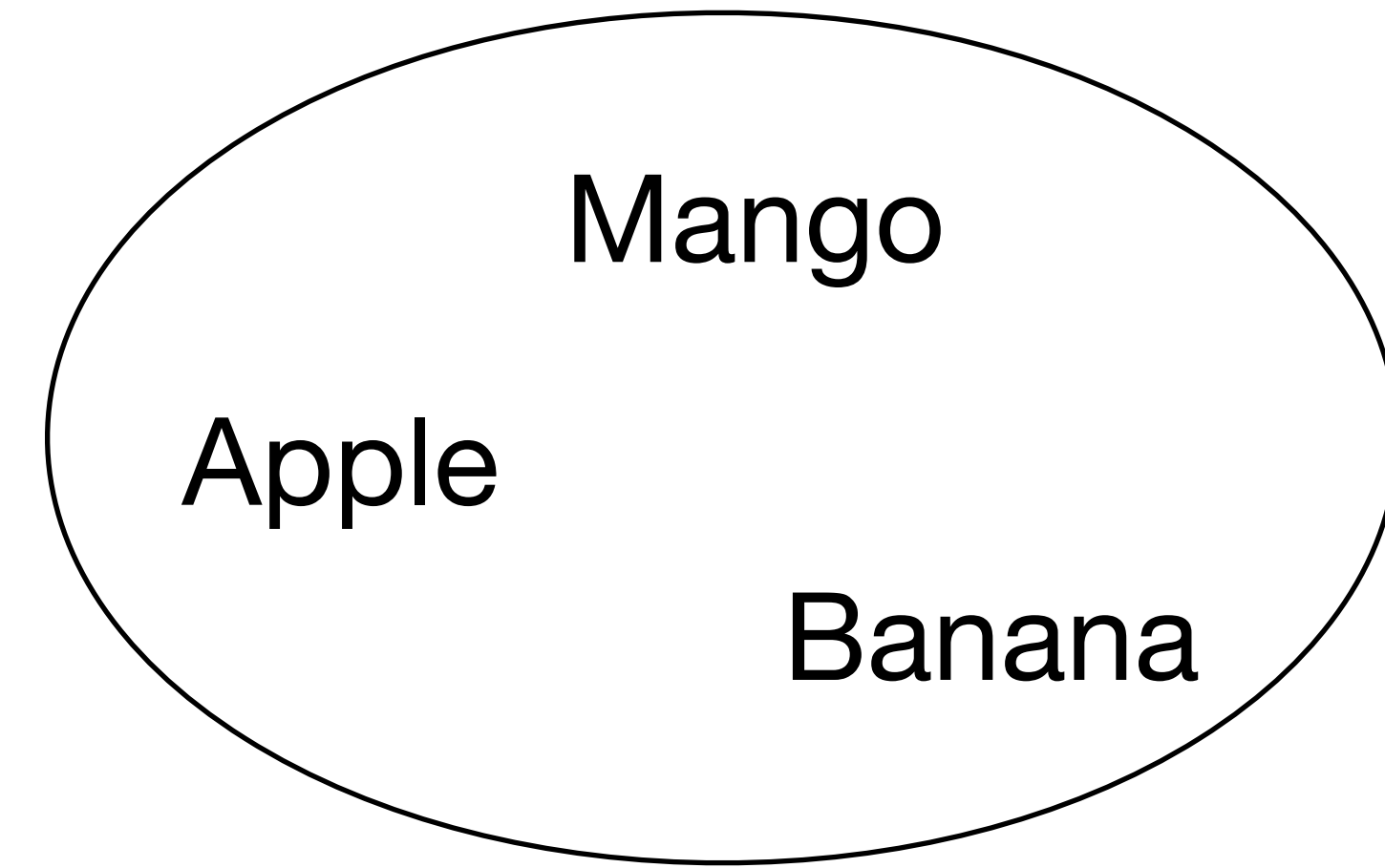- Collection of distinct elements
- $1 \in \{1,2,3\}$ and $4 \notin \{1,2,3\}$
- $\{1,2\} \cap \{2,3\} = ?$
- $\{1,2\} \cup \{2,3\} = ?$
- $\{1,2\} \setminus \{2,3\} = ?$
- $\mathcal{P}(\{1,2,3\}) = ?$




$S = \{1, 2, 3\}$

Relation

$a R b$

Domain (A) Codomain (B)

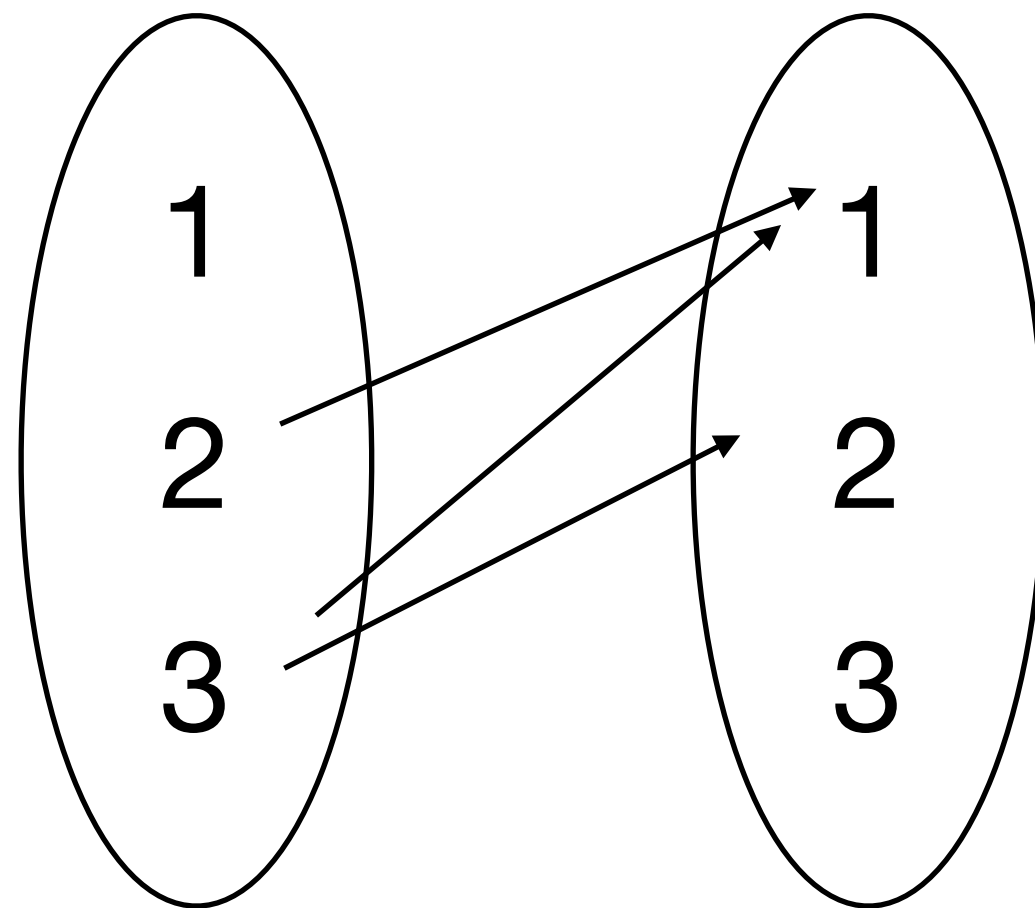


$a > b = \{(3, 1); (3, 2); (2, 1)\}$

- Reflexive relation: $(a R a)$
- Symmetric relation: If $(a R b)$ then $(b R a)$
- Transitive relation: If $(a R b)$ and $(b R c)$ then $(a R c)$
- Equivalence relation is reflexive, symmetric, transitive
- Analyse: $(a > b)$, $(a \geq b)$, $(a = b)$, $(b = 3)$, Cartesian product: $A \times A$

Function

$$b = F(a)$$

Domain (A) Codomain (B)


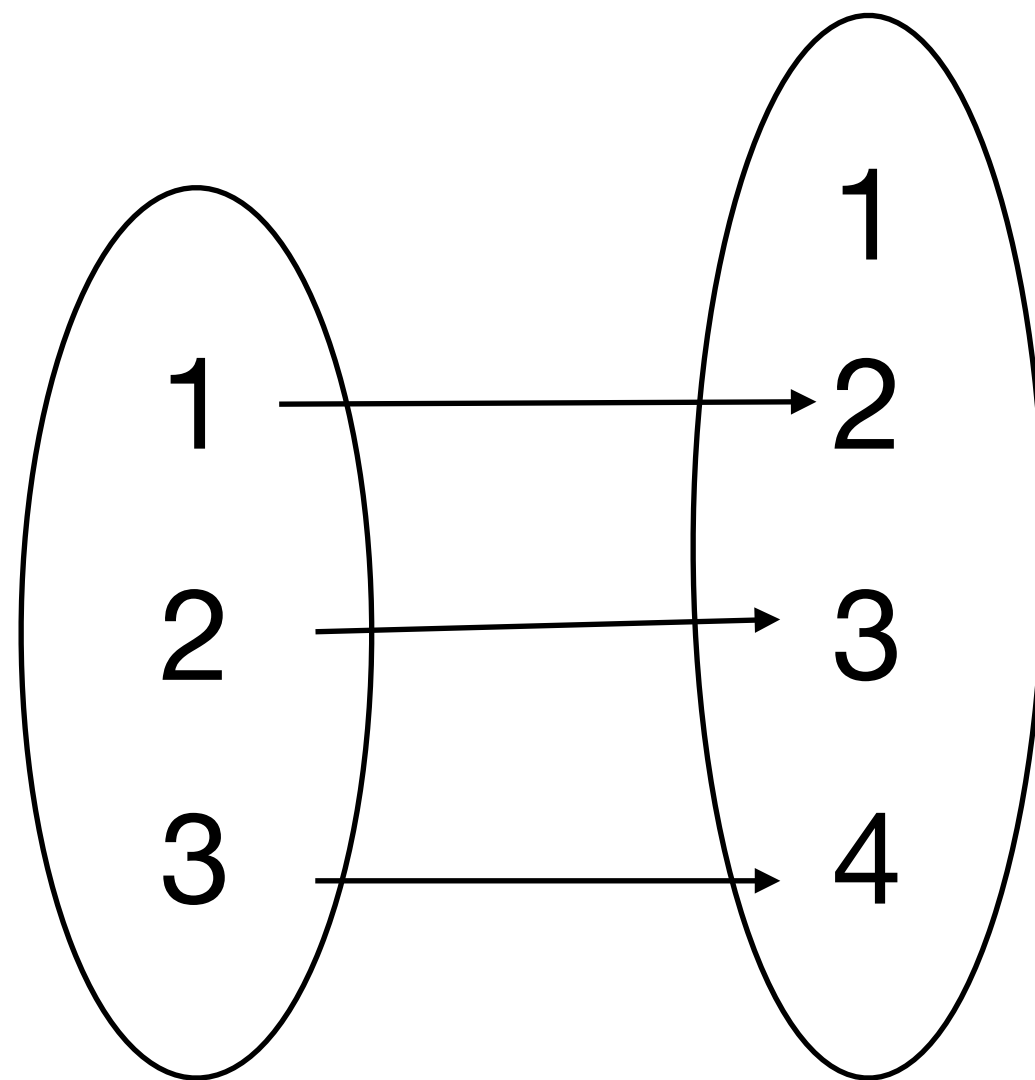


$$b = a + 1 := \{(1, 2); (2, 3); (3, 4)\}$$

- Function is a relation where *each* element in the Domain maps to *exactly one* element in Codomain
- For the given Domain, Codomain:
 - Are following relations functions?
 $a > b$, $a = b$, $b = 3$
 - How many functions are possible?

Unary operators

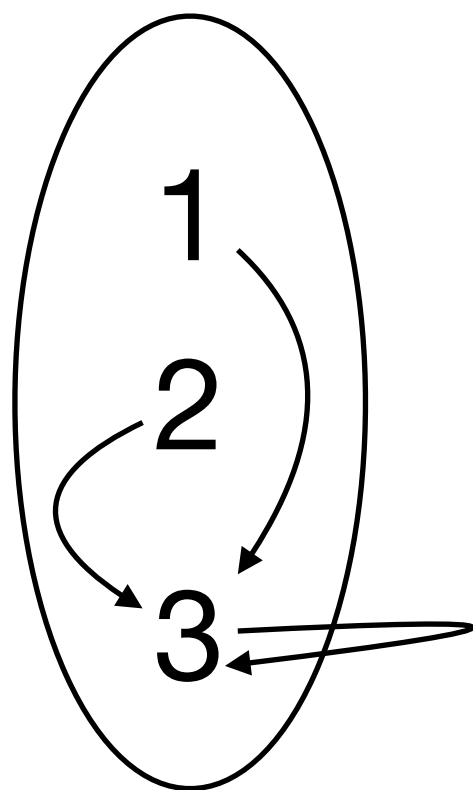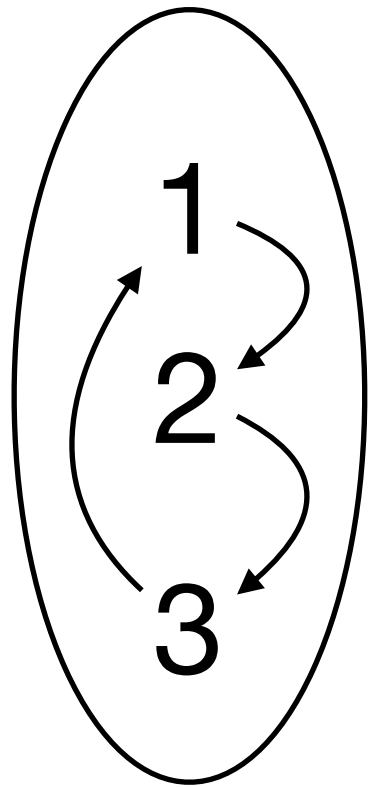- When domain and codomain are identical, a function is also called a *unary operator*.
 - $b = (a + 1) \% 3; b = 3; \dots$
- How many unary operators are possible for the given set?



Binary operators

$a \text{ op } b = c$. $a, b, c \in S$

- Say $a, b \in \mathbb{N}$ (natural numbers). Which of the following are binary operators?
 - Addition +
 - Subtraction -
 - Multiplication *
 - Division /
- What if $a, b \in \mathbb{R}$ (real numbers) or $\mathbb{Q}$ (rational numbers) or $\mathbb{Z}$ (integers)?

Binary Operator Properties

- Commutative: $\forall x, y \in S : x \square y = y \square x$
- Associative: $\forall x, y \in S : (x \square y) \square z = x \square (y \square z)$
- Identity element: $\exists e \in S : \forall x \in S : e \square x = x \square e = x$
- Inverses: $\forall x \in S : \exists y \in S : x \square y = e$
- Distributive: $\forall x, y, z \in S : x \square (y \diamond z) = (x \square y) \diamond (x \square z)$

Binary Operator Properties


- Commutative
 - Associative
 - Identity element
 - Inverses
 - Distributive
- What about $+$, $-$, $*$, $/$ on real numbers?
 - What about set operators $\cap$, $\cup$, $\setminus$ on a power set?

Semiconductor basics

Appendix A

Silicon crystal

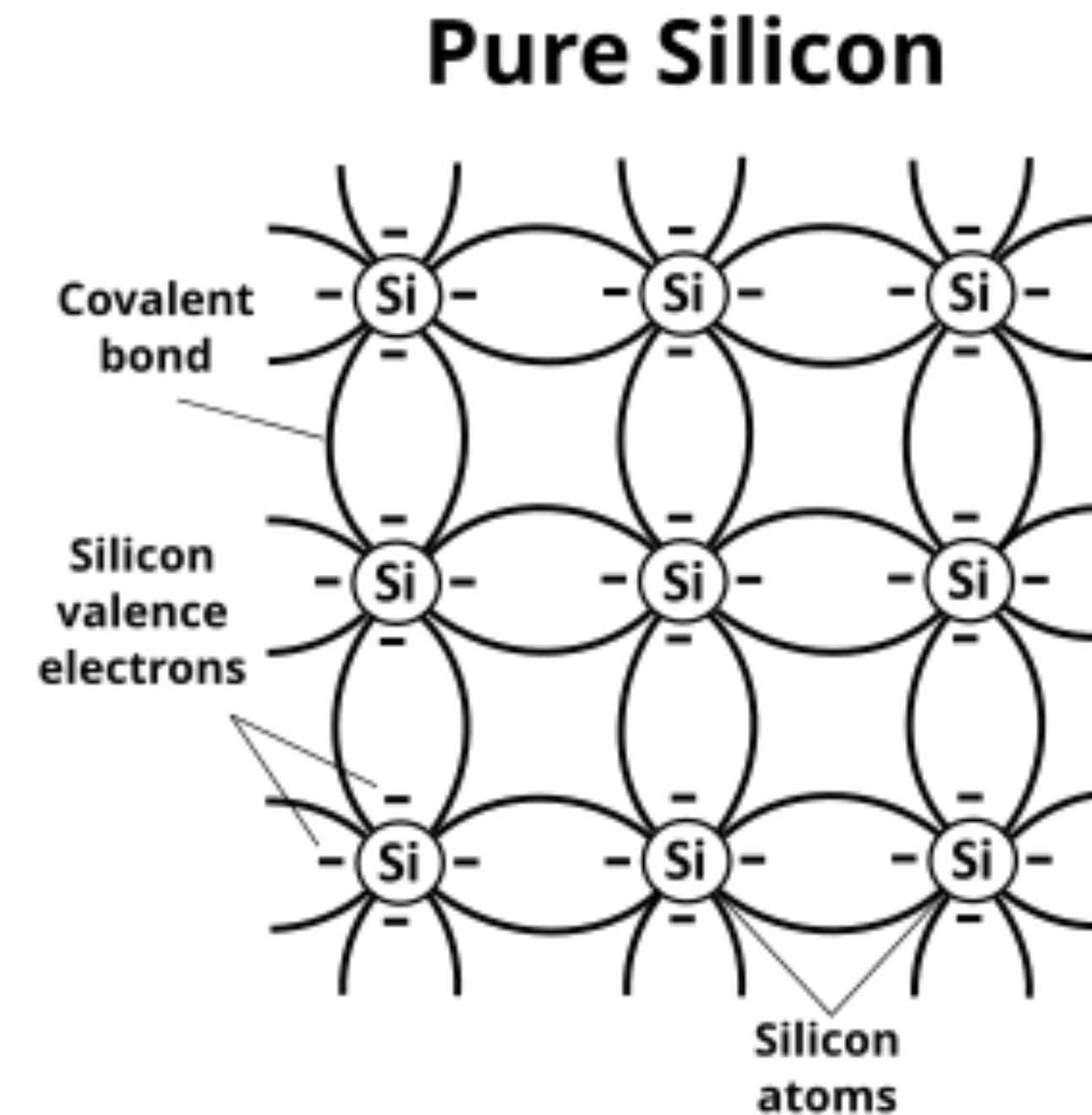- Every silicon atom shares its four valence electrons with its four nearest neighbours
- No free electrons to move with an electric field




Periodic table of elements

		Some elements near the dashed staircase are sometimes called <i>metalloids</i>																		
Nonmetals		1											2							
		H											He							
Metals	2	3	4											5	6	7	8	9	10	
		Li	Be											B	C	N	O	F	Ne	
	3	11	12											13	14	15	16	17	18	
		Na	Mg											Al	Si	P	S	Cl	Ar	
	4	19	20											31	32	33	34	35	36	
		K	Ca											Ga	Ge	As	Se	Br	Kr	
	5	37	38											49	50	51	52	53	54	
		Rb	Sr											In	Sn	Sb	Te	I	Xe	
	6	55	56	La to Yb	71	72	73	74	75	76	77	78	79	80	81	82	83	84	85	86
		Cs	Ba		Lu	Hf	Ta	W	Re	Os	Ir	Pt	Au	Hg	Tl	Pb	Bi	Po	At	Rn
	7	87	88	Ac to No	103	104	105	106	107	108	109	110	111	112	113	114	115	116	117	118
		Fr	Ra		Lr	Rf	Db	Sg	Bh	Hs	Mt	Ds	Rg	Cn	Nh	Fl	Mc	Lv	Ts	Og
		s-block (plus He)		f-block	d-block										p-block (excluding He)					
				Lanthanides	57	58	59	60	61	62	63	64	65	66	67	68	69	70		
					La	Ce	Pr	Nd	Pm	Sm	Eu	Gd	Tb	Dy	Ho	Er	Tm	Yb		
				Actinides	89	90	91	92	93	94	95	96	97	98	99	100	101	102		
					Ac	Th	Pa	U	Np	Pu	Am	Cm	Bk	Cf	Es	Fm	Md	No		


Doping

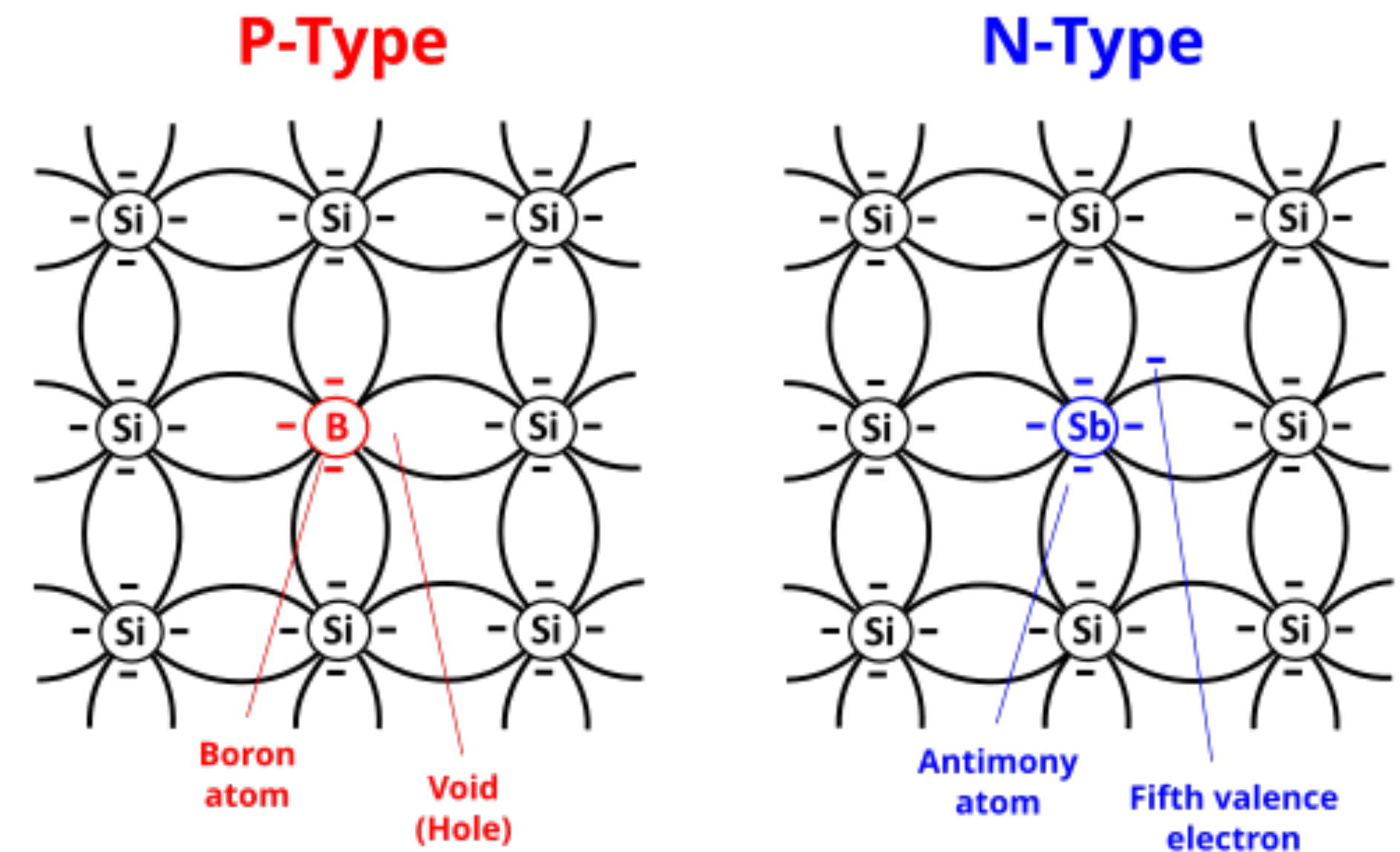- Dopants fit easily into the silicon crystal
- P-type dopants (Boron/Gallium) have one less electron (valency of 3)
- N-type dopants (Antimony/Phosphorous) have an extra electron (valency of 5)





Extra electrons/holes can flow current

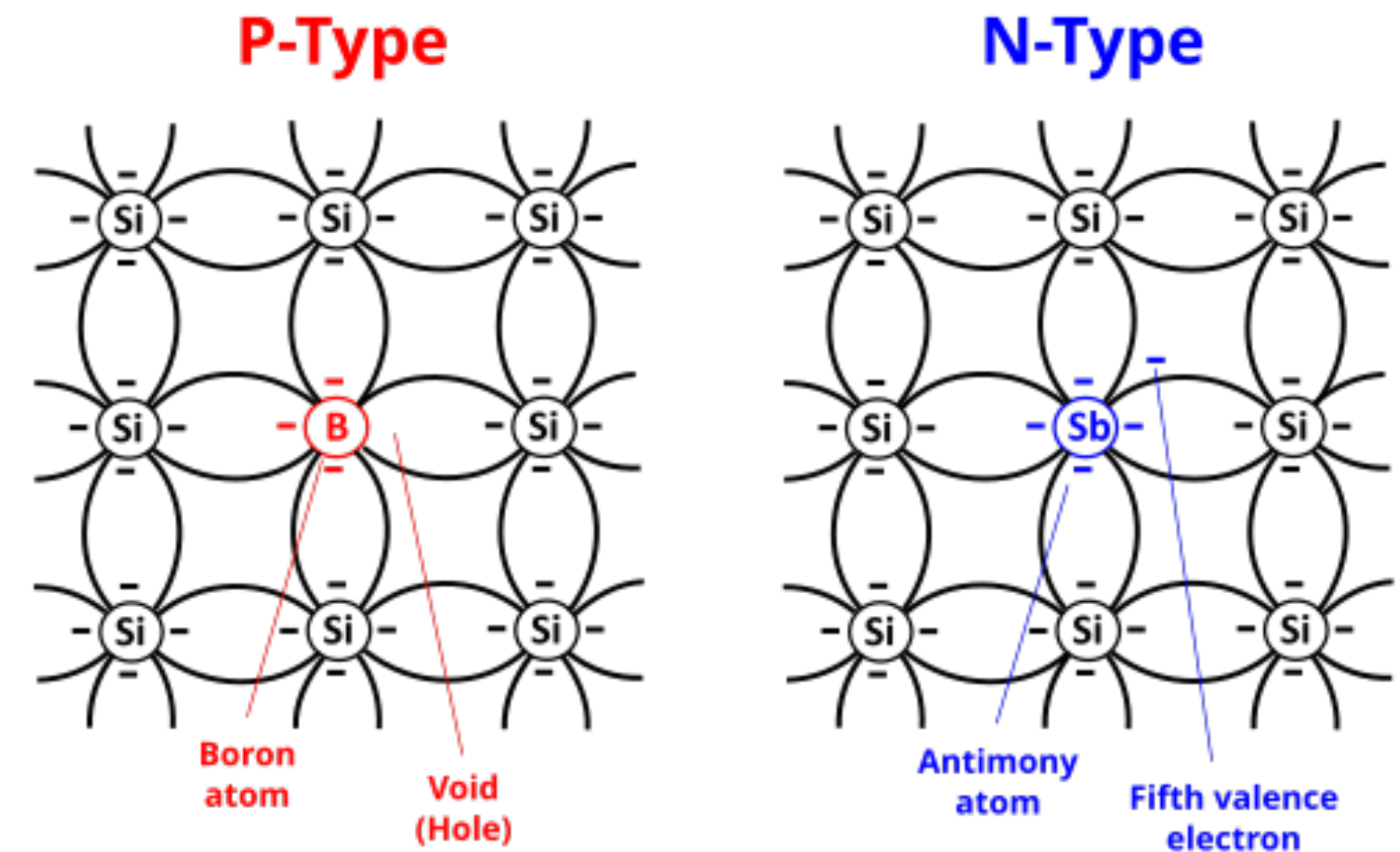- Current moves in the opposite direction of electrons
- Current moves in the same direction as holes
- Metal-Oxide Semiconductor (MOS) either flow holes or electrons





p-channel transistor

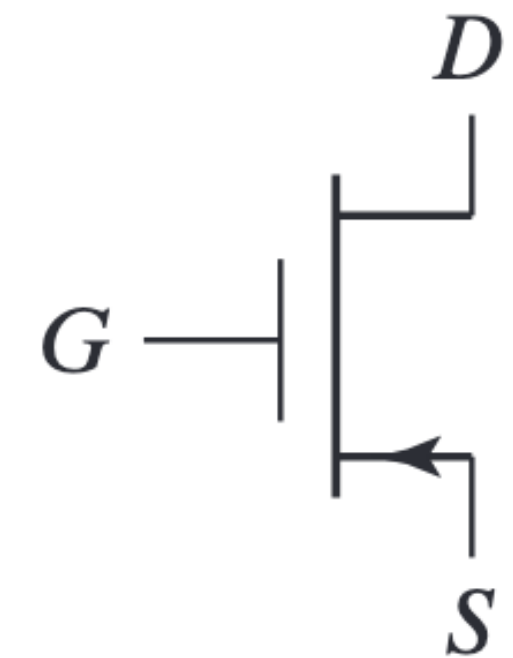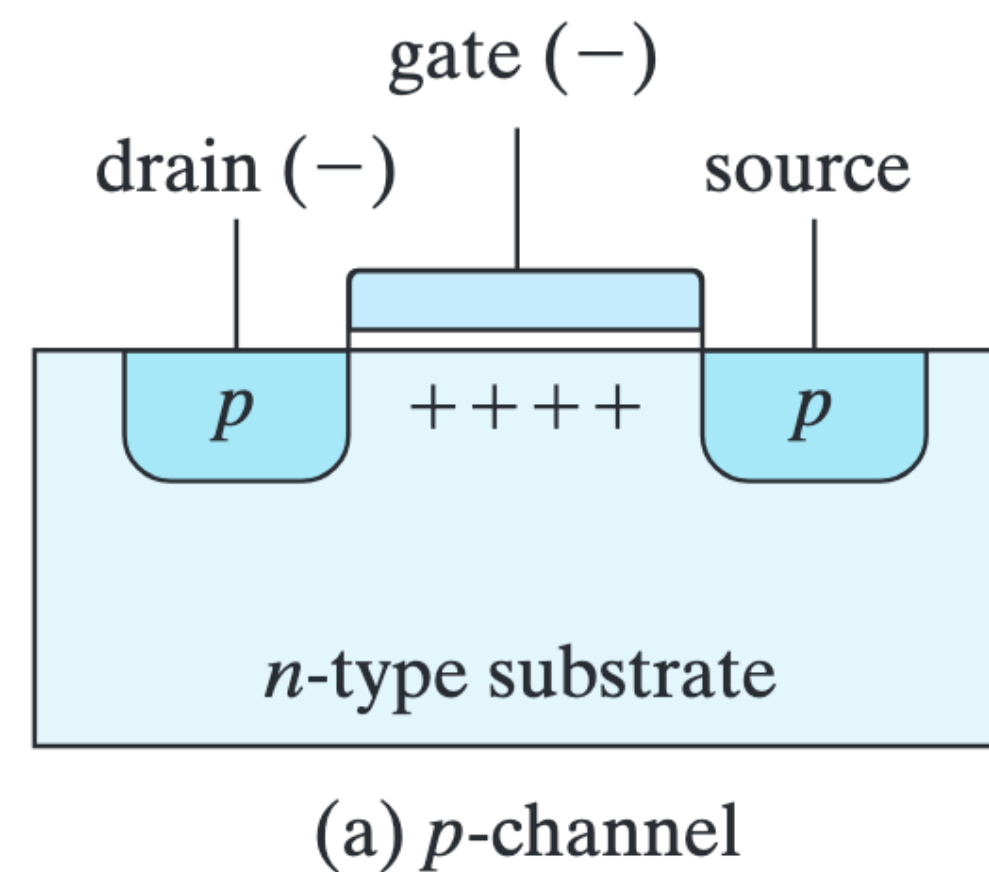- In p-channel transistor, when gate-to-source voltage $>$ threshold ($-2V$), no current flows.
- Holes flow from source to drain
- Current flows from source to drain





n-channel transistor

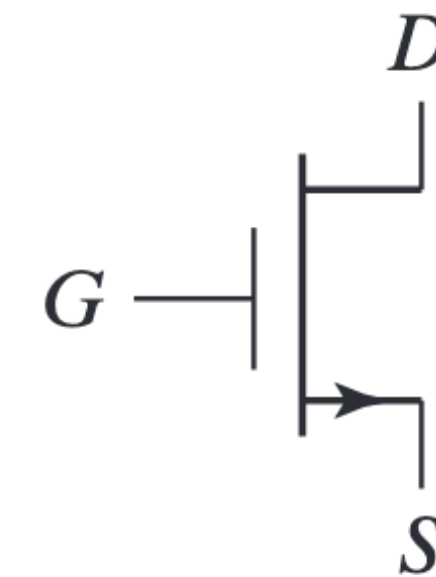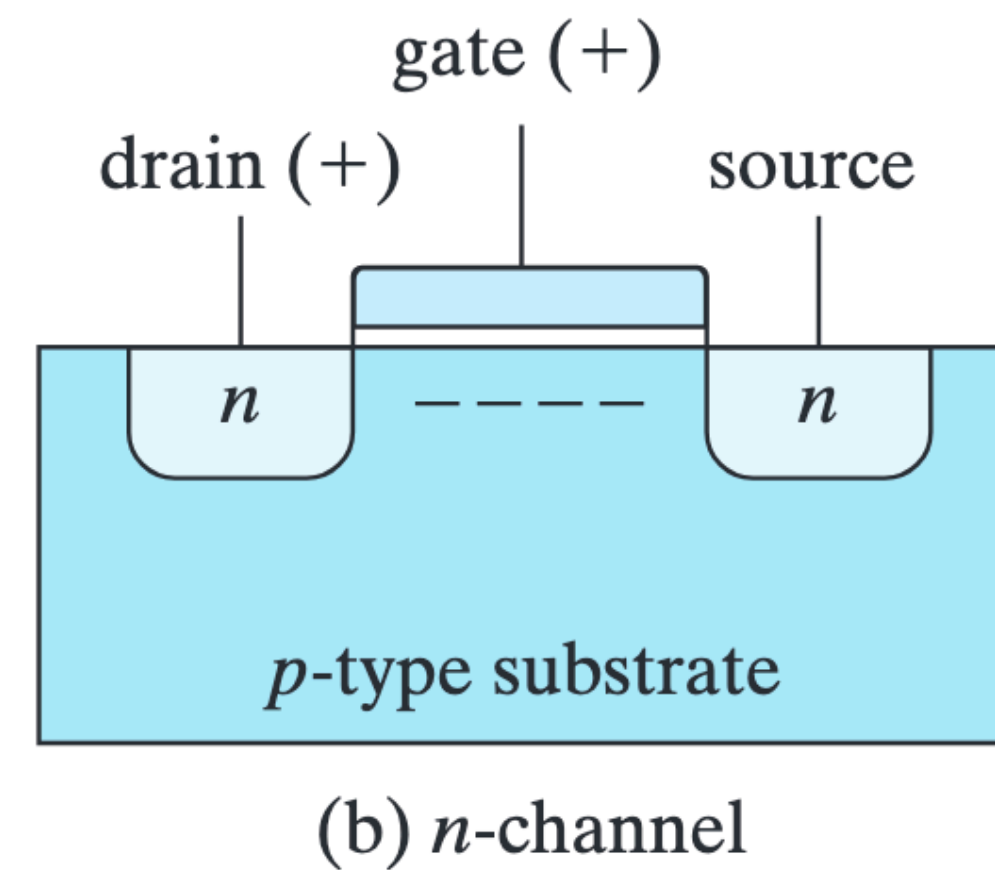- In n-channel transistor, when gate-to-source voltage $<$ threshold ($2V$), no current flows.
- Electrons flow from source to drain
- Current flows from drain to source



MOS device as a resistor

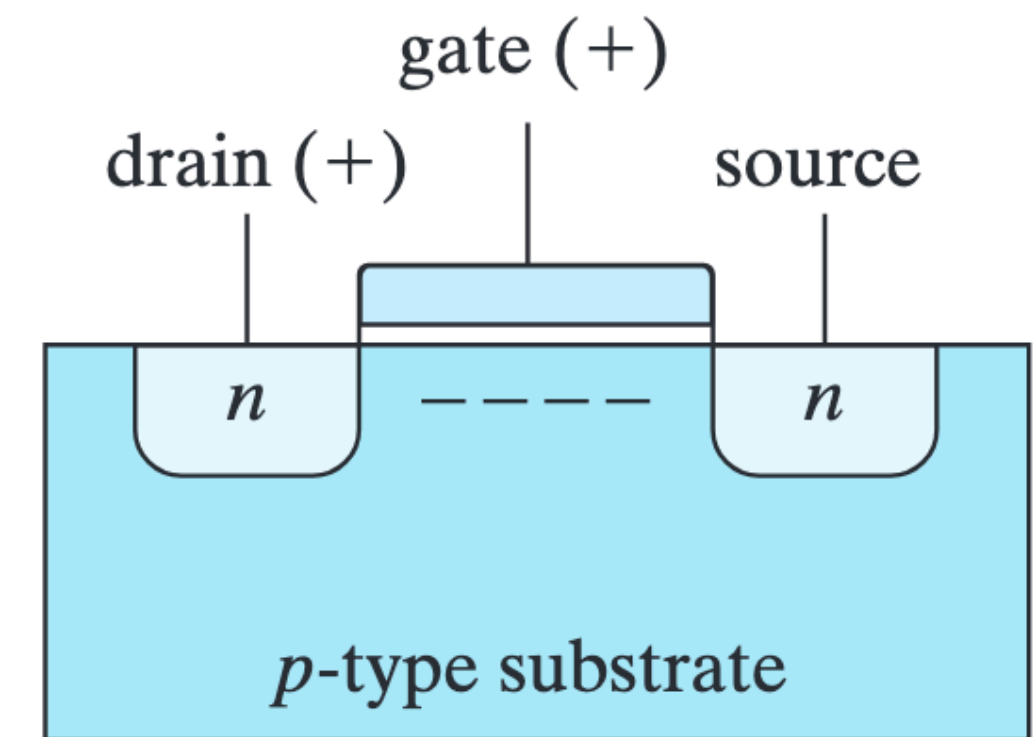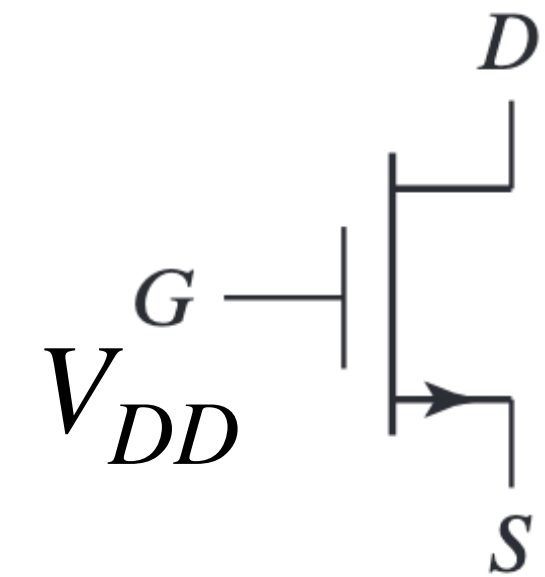
- A resistor is obtained from the MOS by *permanently biasing* the gate terminal for conduction
- In n-channel device, when gate-to-source voltage $<$ threshold ($2V$), no current flows
- In n-channel resistor, gate-to-source voltage is always $>$ threshold
- Different resistor value can be constructed during manufacturing by fixing the channel length and width of the MOS device



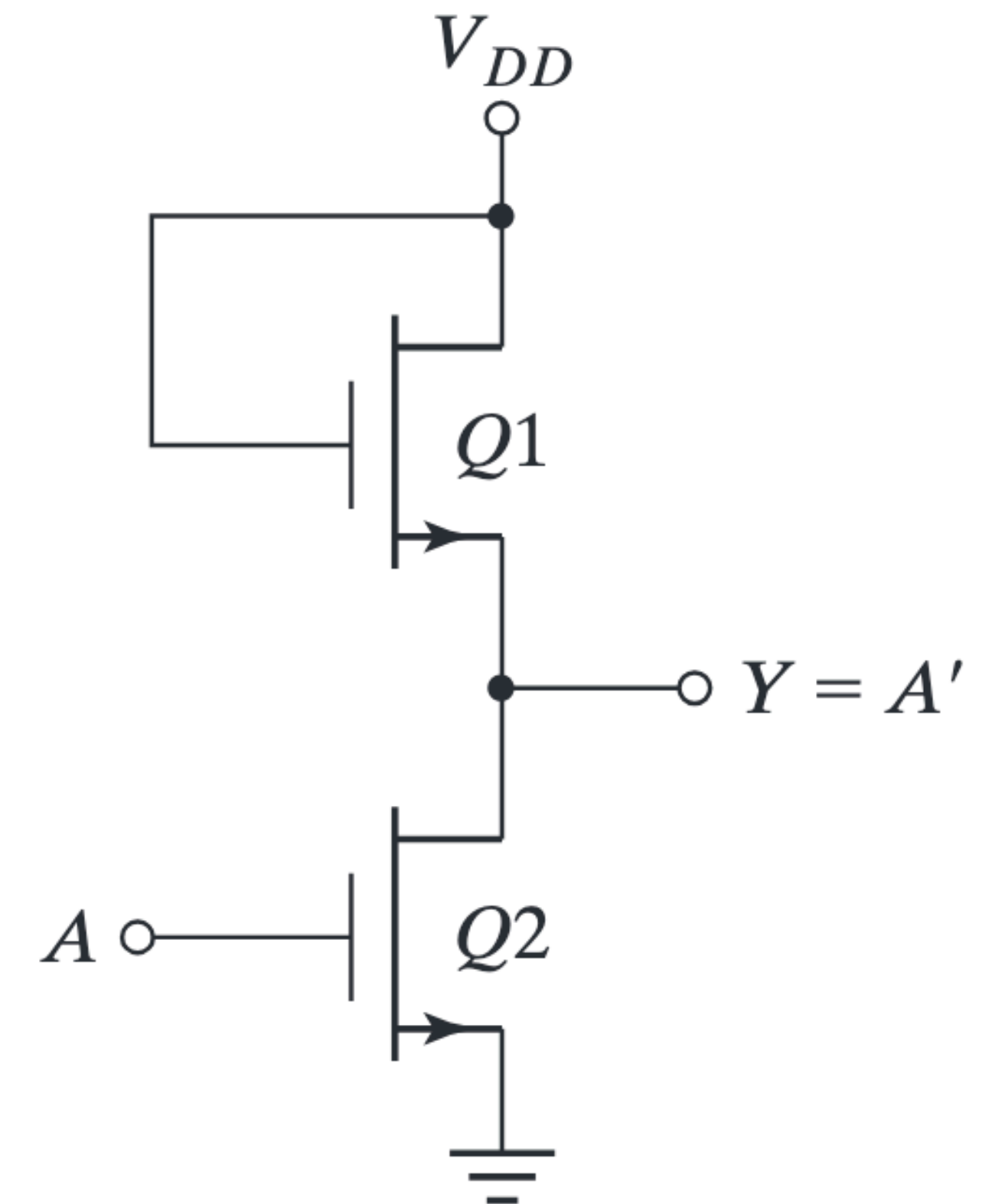(b) *n*-channel

n-channel Inverter



- In n-channel device, when gate-to-source voltage $<$ threshold ($2V$), no current flows.
- Q1 acts as a load resistor (always in the conduction state). Q2 as the active device (encodes the logic of the circuit)
- When $A < V_T$, Q2 turns off. Since Q1 is always on, $Y > V_T$
-



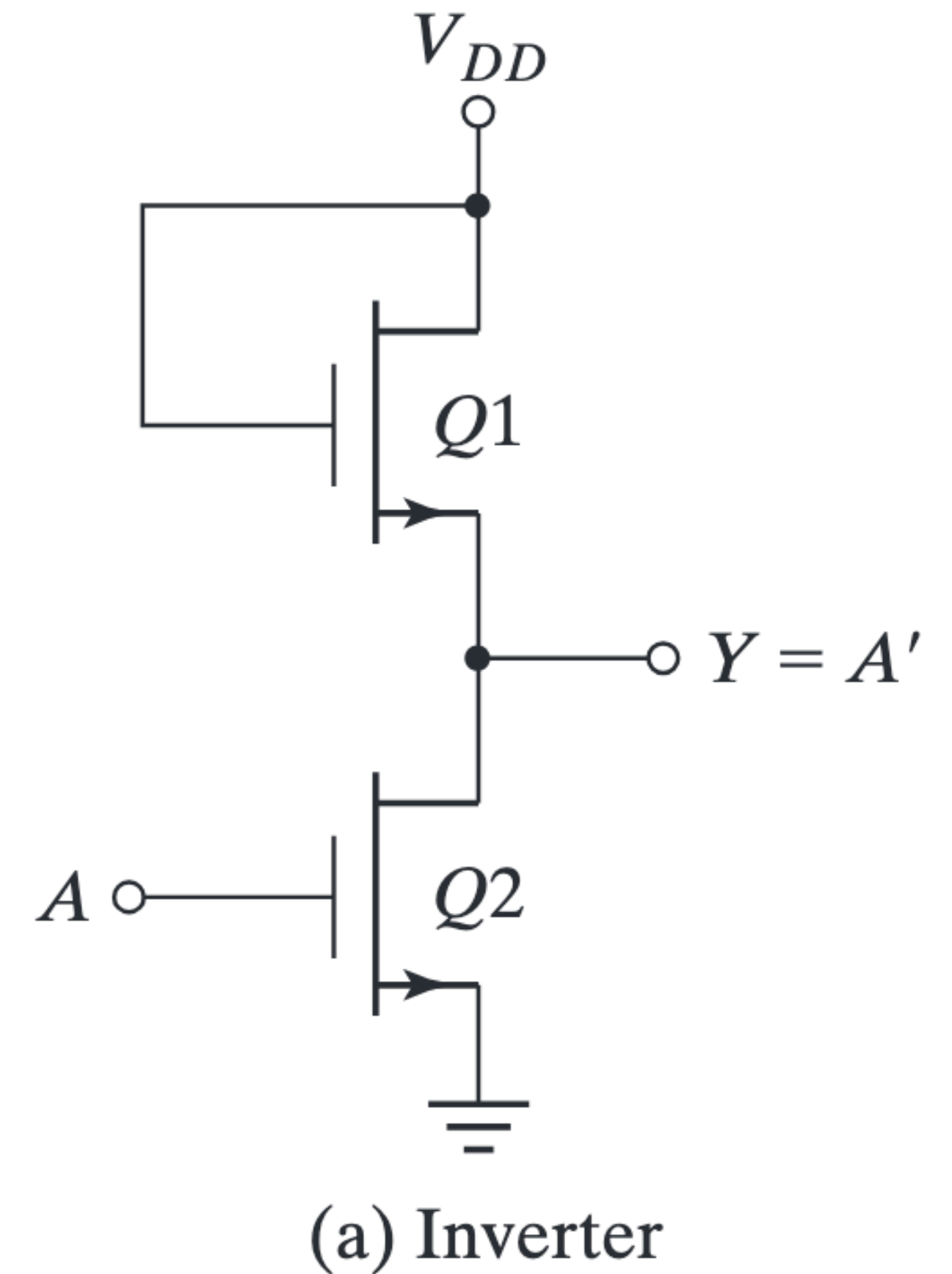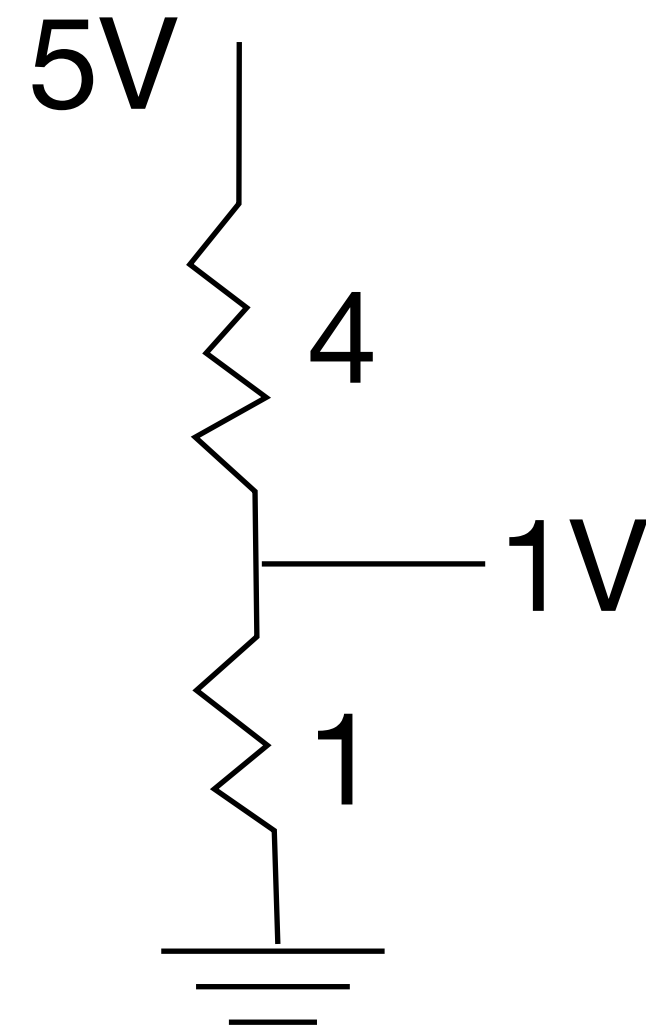(a) Inverter


n-channel inverter (2)

- When $A > V_T$, Q2 turns on. Current flows from V_{DD} via Q1 and Q2. Resistance of Q2 is less than resistance of Q1 to ensure that $Y < V_T$




n-channel NAND gate

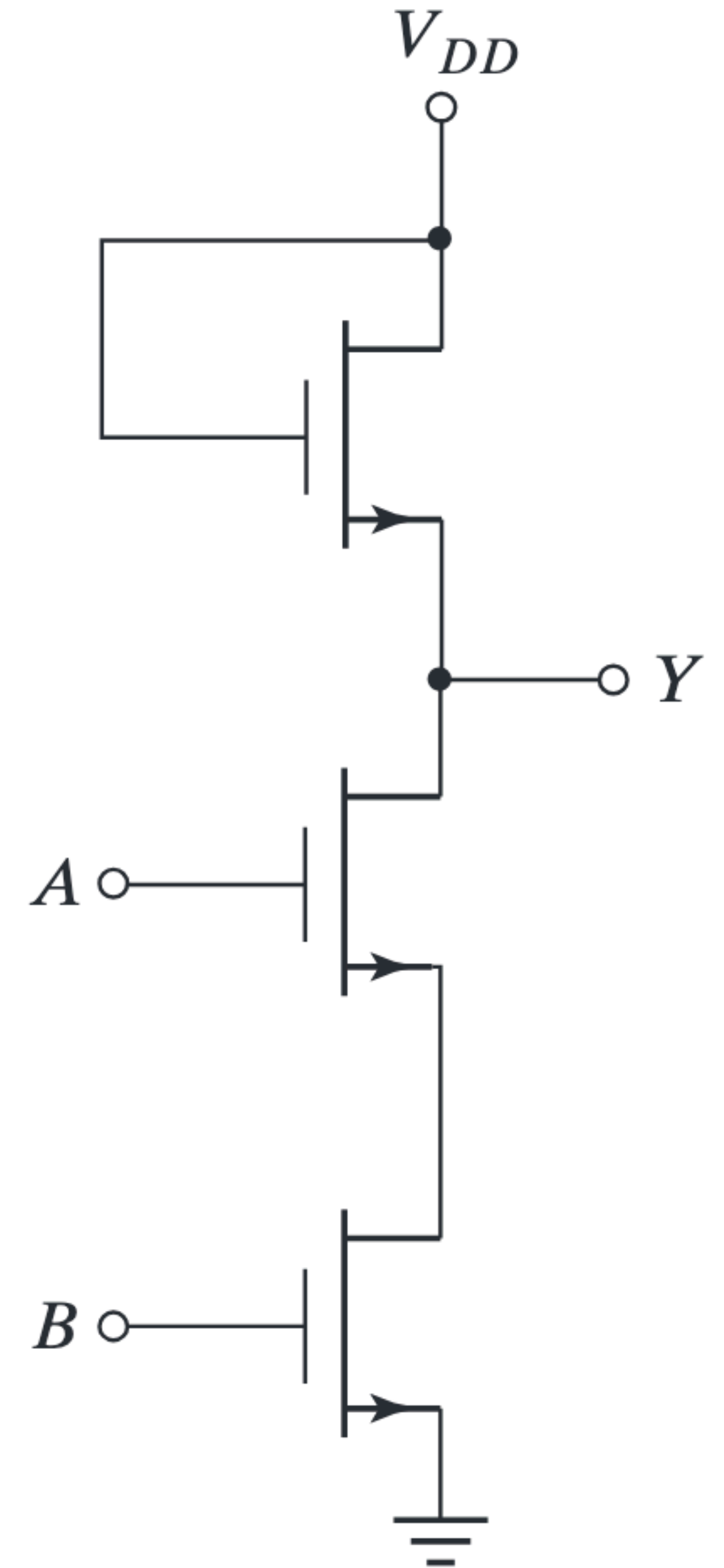- When $A > V_T$ and $B > V_T$, $Y < V_T$
- When $A < V_T$ and $B > V_T$, $Y \approx V_T$
- When $A > V_T$ and $B < V_T$, $Y \approx V_T$
- When $A < V_T$ and $B < V_T$, $Y \approx V_T$



n-channel NOR gate

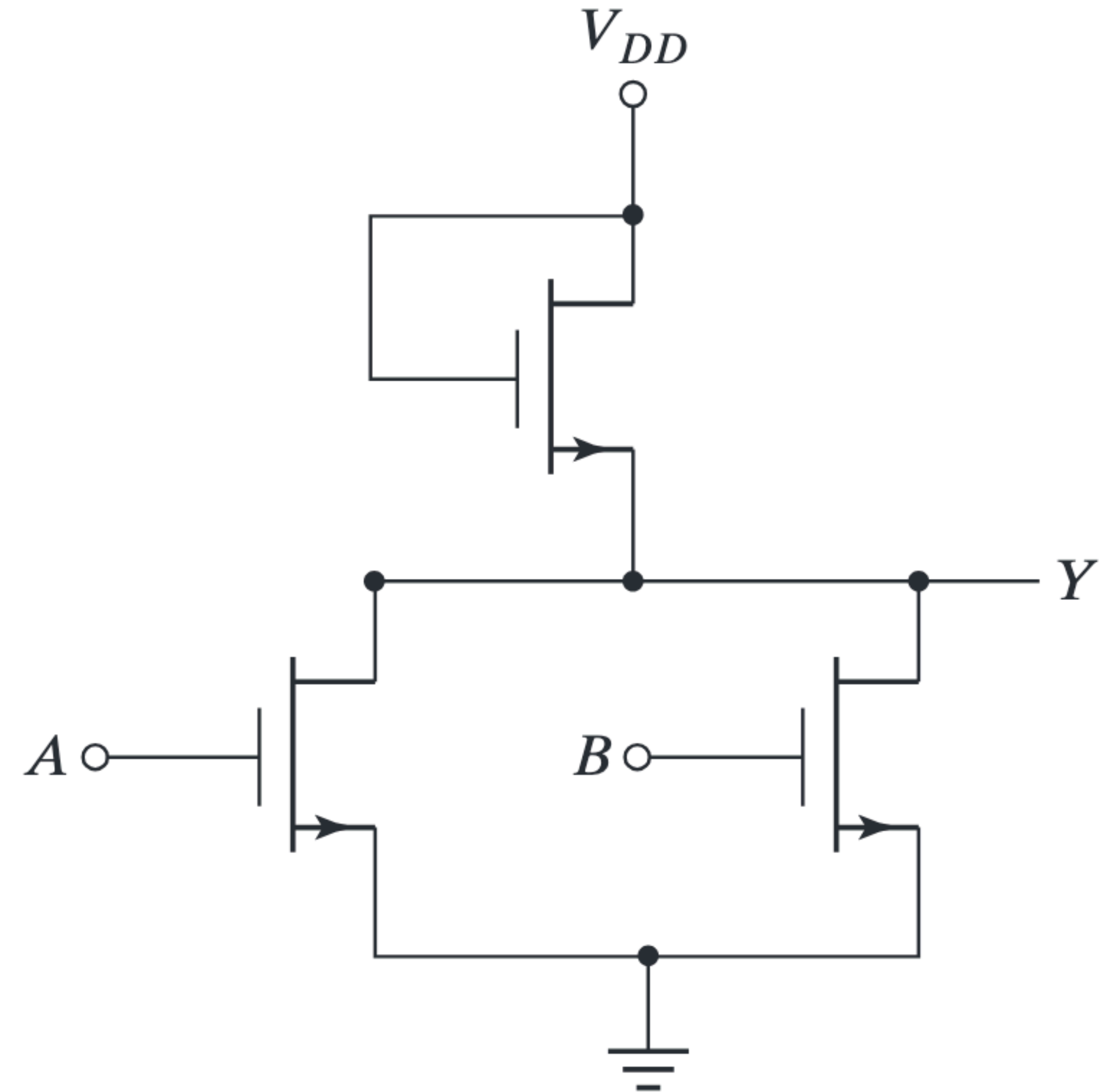- When $A > V_T$ and $B > V_T$, $Y < V_T$
- When $A < V_T$ and $B > V_T$, $Y \approx V_T$
- When $A > V_T$ and $B < V_T$, $Y \approx V_T$
- When $A < V_T$ and $B < V_T$, $Y \approx V_T$



p-channel circuits


- Inverter?
- NAND gate?
- NOR gate?

Complementary MOS (CMOS)

- Both n-channel and p-channel transistors can be fabricated on single silicon crystal
- CMOS circuits contain both types of transistors
- Source terminal of p-channel transistor is at V_{DD} (usually +5V). Source terminal of n-channel transistor is at GND

Inverter revisited

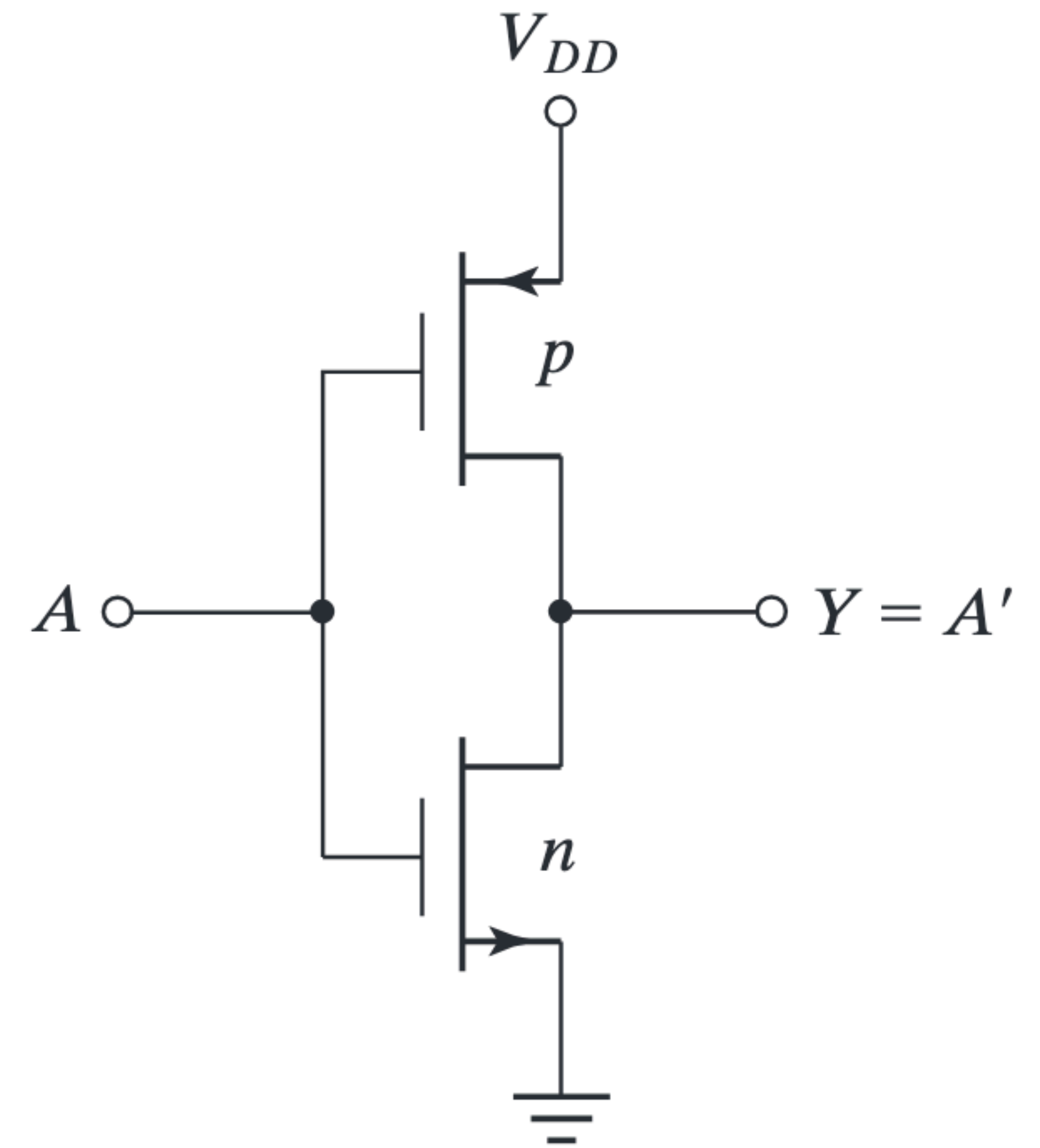- n-channel MOS conducts when its gate-to-source voltage is positive.
- p-channel MOS conducts when its gate-to-source voltage is negative.
- Neither device conducts when its gate-to-source voltage is zero.
- When $A = V_{DD}$, $Y = ?$
- When $A = \text{GND}$, $Y = ?$



(a) Inverter